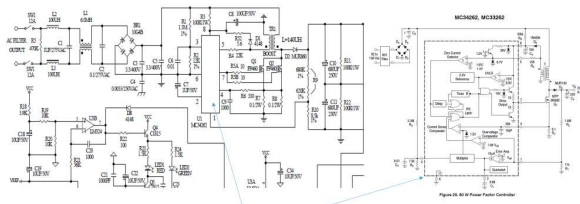



Our last meeting 9th July 2024

Testing basic components and reading schematics with Keith VK2KQB

Reading Schematics
Finding components




Using DATA SHEETS of components is handy

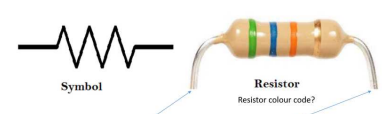

Symbol

Resistor
Resistor colour code?

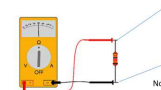

No colours left, Schematic?
Work out wattage?

Try to measure out of circuit if the reading you get is unexpected.

Note: Resistors with high voltage and high power normally fail before others

The presentation was based on basic testing and fault finding of components, including the use of low cost in the shack test equipment.




Asking question time 😊



You do WHAT!!!


Basic Component Testing BJT

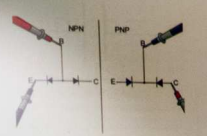

OUT OF CIRCUIT TESTING
NPN positive to Base, PNP negative to Base

- Germanium = 0.2 to 0.3 Volts
- Silicone = 0.6 to 0.7 Volts
- PNP or NPN collector to emitter no readings

Electronic Schematic Diagram

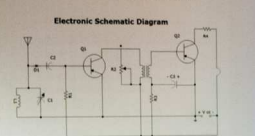


NPN Transistor
Collector
Base
Emitter

PNP Transistor
Collector
Base
Emitter

N Never
P Points
N IN

P Points
N IN
P Permanently

Basic Component Testing MOSFET

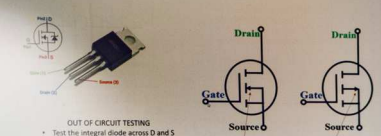

OUT OF CIRCUIT TESTING

- Test the integral diode across D and S
- Test the other way should be open circuit
- Charge the GATE with positive lead, neg on Source
- Should have a low reading between D and S
- Discharge by shorting Gate to Source

Same test for P channel just reverse polarity

N-Channel MOSFET
P-Channel MOSFET

Tips on testing BJT, Jfet and Mosfet transistors using simple multimeters



Setting up the meters and power supplies , checking parts and getting down to the nitty gritty 😊



It was good to see members getting involved with the component testing, great evening was had by all.

A catchup with mates afterwards, always spare biscuits to go round.

If you require more information about the presentation, please send Keith an email at iars.keithb@gmail.com

NEXT MEETING



The next meeting will be the society's AGM, where a new committee will be elected for the year moving forward.

All committee positions will be vacated with some committee members remaining available for re-election.

Please ensure that if you are nominating for a position that the nominations are submitted to the secretary at least 1 week before the meeting.

Current IARS Committee members

- President Tony Stone VK2TS
- Vice President Rob McKnight VK2MT
- Treasurer John Lawler VK2EJL
- Secretary Keith Bradshaw VK2KQB
- Committee member Simon Ryan VK2KU
- Committee member Mal St Clair VK2DXM
- Committee member Simon Ferrie VK2XQX
- Committee member Dan Demaagd VK2FDSD
- Committee member Shane Sorgsepp VK2HCO

The IARS would like to thank the committee members for all the work they did for the society during the last 12 months, hopefully they may want to come back and serve for another year, if not are you ready for the challenge?



Please find nomination forms on the website or print off the next page of the propagator if you or know of someone who would like to serve in the IARS committee for 2024/2025

The NEW IARS committee will be proposing the finalisation of the new updated constitution which will be sent to all members prior to the AGM.

As always there will be the usual chinwag with a nice warm cuppa of your favourite brew, including something nice to nibble on.



ILLAWARRA AMATEUR RADIO SOCIETY (INC)

PO Box 1838, Wollongong NSW 2500

Web: www.iars.org.au Email: iars@iars.org.au

NOMINATION FORM

I, (name)

of(address)

being a member of the Illawarra Amateur Radio Society, hereby nominate for the position described below. If I am successfully elected as a committee member I agree to be bound to the rules and constitution of the Illawarra Amateur Radio Society and serve accordingly.

Nominated position:

.....
Signature of nominee	Call sign	Date

I, Call sign:

being a member of the Illawarra Amateur Radio Society, second this application.

.....
Signature of seconder	Call sign	Date

Nomination forms must reach the secretary by the first Tuesday in August |

I, accept the nominated position.

.....
Signature of the elected committee member	Date



Affiliated with the
Wireless Institute of Australia

VK2RMP – VK2RUW – VK2AMW

Membership fees

We still have many membership payments outstanding and are hoping that we can get this all settled before the next meeting. The IARS membership fees are still one of the **lowest** at **\$25.00 normal, \$20 concession**. This relates to \$2.20 per month, for 11 meetings (less than the price of a cup of coffee)



Your membership fees keep your club operational, please support your club.

All monies from our interest on investment, donations and membership fees goes to support the club with **Public liability insurances, Repeater maintenance, Repeater site fees, Blue scope meeting hall rental, IARS call signs with the ACMA, Coffee, tea & refreshments, Outings & picnics and Christmas dinner.**

Excellent value for money!!!!

We want to thank the members who have paid membership and the extra donations we received this year, much appreciated.

To make payments you could either pay John VK2EJL at the next meeting OR use the IARS bank account (info below),

please add your call sign or name with the payment,

Bank: IMB Wollongong
Account name: Illawarra Amateur Radio Society
BSB: 641800
Account number: 100023291



Please join us in welcoming our new members:

- **Mike Hayes VK2BIO**
- **David Wilson VK2AAW**
- **Handyn Kerr VK2LUV**

Welcome to the IARS family



LOOKING FOR SOMETHING to SWAP, BUY, SELL, an OLD PART

Parts you may need for repairs or some radio gear you no longer need that could go to a new home.....?

Email jars.keithb@gmail.com

Kenwood TS-820s looking for a new home, contact Keith jars.keithb@gmail.com.au if you are interested in buying this great transceiver



Electronic component and service suppliers

Need a quick PCB in a hurry to put that latest project on, JLCPCB

https://jlcpcb.com/?from=VGB&gad=1&gclid=EAIaIQobChMInOCo_9K1gQMVGw17Bx3qLAN0EAAYASAAEgLOV_D_BwE

element14
AN AVNET COMPANY

<https://au.element14.com>



<https://au.rs-online.com/web/>



<https://au.mouser.com>



<https://www.digikey.com.au>

Minikits

<https://www.minikits.com.au>



<https://core-electronics.com.au>



<https://www.wagneronline.com.au>



<https://littlebirdelectronics.com.au>



<https://www.altronics.com.au/virtualtour/nsw/auburn/>



<https://amateurradiosupplies.com.au>



<https://www.elitecommunications.com.au/mobile-communications-category/communication-equipment/amateur-radio/amateur-radio-accessories/>



<https://www.vkradio.com.au>



<https://dxing.com.au>

If you know of a good supplier of electronic stuff or services 😊, please share it with us so we can all enjoy.

Send information to jars.keithb@gmail.com and we will publish it in the next propagator.



Share it with us, this could be suggestions, technical ideas, circuit diagrams, IARS community projects, pictures of your latest shack project, in fact **ANYTHING of interest**

Let us know by return email iars.keithb@gmail.com

If you have some IARS related pictures or information that we can put on the **IARS website**, please let us know and we can get that happening.


.....

6m Flowerpot

As we covered the 10m flowerpot last month, we thought it would be a good idea to cover a 6m flowerpot.

There is plenty of information out there all based on the original design by is a great design by the late John Bishop VK2ZOI.

6 Meter Flower Pot

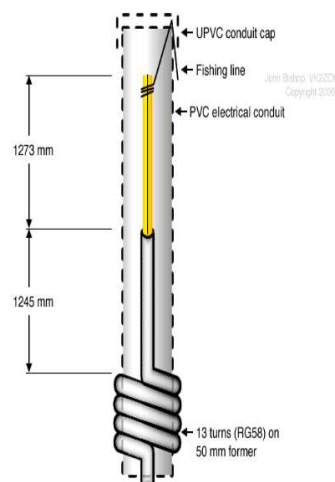

The 'Flowerpot' antenna is an end-feed, coaxial dipole antenna designed by **John Bishop VK2ZOI**.

It is made using a single length of standard RG58c/u coaxial cable and has a resonant choke wound in the coax immediately below the lower element to provide RF isolation between the antenna and the feed line. The antenna is enclosed in a length of PVC pipe to protect it from the elements.

The antenna performs very well and the construction is simple, meaning almost anyone can construct one and have it running in an afternoon. All you need is some RG58c/u coax and a length of PVC pipe.

IARS's very own Simon VK2XQX is looking at a possible project with a complete kit to include the 50mm winding former. Watch this space

As there are so many options to build and test your very own flowerpot antennas, we cannot cover it all here, please use these handy links:

<https://vk2zoi.com/articles/half-wave-flower-pot/>

<https://vk2idl.com/index.php/6m-flowerpot-antenna/>

<https://www.emdrc.com.au/coax-ant-for-6m/>

[https://barcvk4ba.com.au/assets/projects/flowerpot_antenna/VK4PK My 6m Flowerpot Antenna-v1.0.pdf](https://barcvk4ba.com.au/assets/projects/flowerpot_antenna/VK4PK_My_6m_Flowerpot_Antenna-v1.0.pdf)

<https://www.lyonscomputer.com.au/Antennas/My-Antennas/Flowerpot/Flowerpot.html>

Good luck and perhaps let us know how you went with your design and if you have anything special to share about your flowerpot project please send it to iars.keithb@gmail.com and we will publish it in future propagators.

XX


Amplifiers! What Class are you?

As amateur radio operators we have often heard of, and use Class A , Class B , Class AB, Class C and even a Class D. However, how about Class E and Class F, I am sure the only time I heard of class F was when one blew up while testing, it was very quickly called class "F". 😊 However, there is a definite move to the lesser-known classes of amplifiers for RF amplification and who is Doherty?


Class - E

Class-E employs a single transistor operated as a switch. The collector/drain voltage waveform is the result of the sum of the DC and RF currents charging the drain-shunt capacitance C_p which is parallel with transistor internal capacitance c_o . In optimum class E, the drain voltage drops to zero and has zero slope just as the transistor turns on. The result is an ideal efficiency of close to 100 %, elimination of the losses associated with charging the drain capacitance in class D, reduction of switching losses, and good tolerance of component variation.

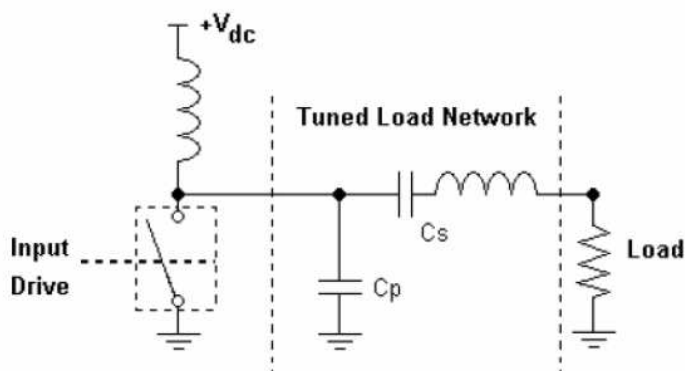The circuit obtains high efficiency by only operating the switching element at points of zero current (on to off switching) or zero voltage (off to on switching) which minimizes power lost in the switch, even when the switching time of the devices is long compared to the frequency of operation



Class-E amplifier

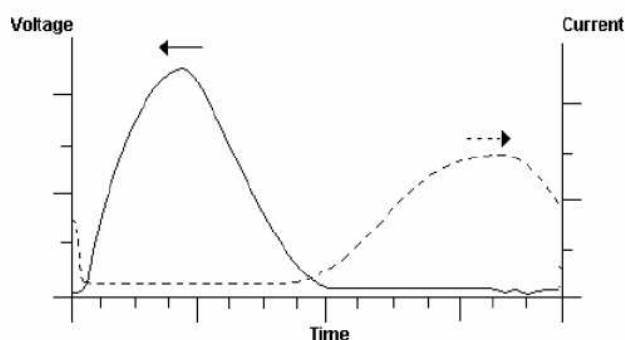


Class-E Voltage and Current waveforms

- A Class-E amplifier will exhibit an upper limit on its frequency of operation based on the output capacitance required for the output matching circuit that produces the waveforms described and shown above.
- Specifically, a Class-E amplifier for optimum efficiency requires an upper limit on capacitance C_s .
- The radio frequency choke (RFC) is large, with the result that only DC current I_{dc} flows through it.
- The Q of the output circuit consisting of L_s and C_s is high enough so that the output current i_o and output voltage v_o consist of only the fundamental component. That is, all harmonics are removed by this filter.
- The transistor behaves as a perfect switch. When it is on, the collector/drain voltage is zero, and when it is off the collector current is zero.
- The transistor output capacitance c_o , and hence C_p , is independent of voltage.
- If a given transistor has an intrinsic capacitance c_o greater than C_{p_max} , it is not useable at the desired frequency. This C_s requirement implies that for high power at high frequencies, higher current densities are required, as the cross-sectional area of the switch corresponds directly to the device's intrinsic capacitance.


The class-E amplifier is frequently cited to have been first reported in 1975. However, a full description of class-E operation may be found in the 1964 doctoral thesis of Gerald D. Ewing. Interestingly, analytical design equations only recently became known.

Class – F

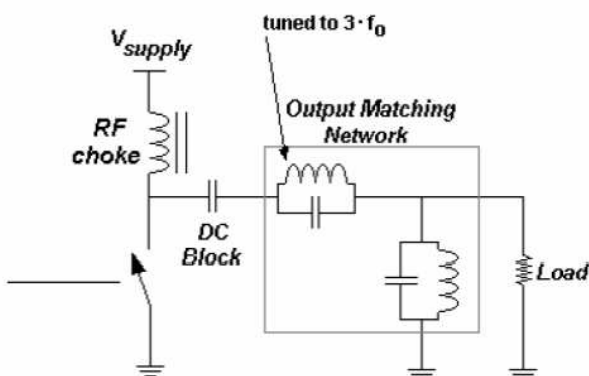Class-F boosts both efficiency and output by using harmonic resonators in the output network to shape the drain waveforms. The voltage waveform includes one or more odd harmonics and approximates a square wave, while the current includes even harmonics and approximates a half sine wave. Alternately (“inverse class F”), the voltage can approximate a half sine wave and the current a square wave



Class-F amplifier

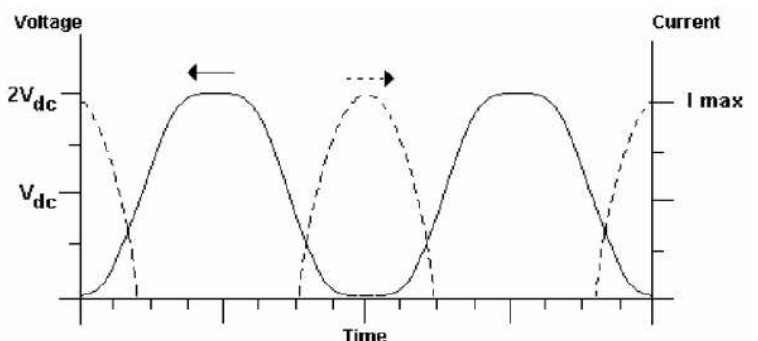


Class-F Voltage and Current waveforms

- The required harmonics can in principle be produced by current source operation of the transistor. However, in practice the transistor is driven into saturation during part of the RF cycle and the harmonics are produced by a self-regulating mechanism similar to that of saturating Class-C. Use of a harmonic voltage requires creating a high impedance (3 to 10 times the load impedance) at the collector/drain, while use of a harmonic current requires a low impedance (1/3 to 1/10 of the load impedance). While Class-F requires a more complex output filter than other PAs, the impedances must be correct at only a few specific frequencies. Lumped-element traps are used at lower frequencies and transmission lines are used at microwave frequencies. Typically, a shorting stub is placed a quarter or half-wavelength away from the collector/drain
- Class-F amplifier designs intentionally squaring the voltage waveform through controlling the harmonic content of the output waveform. This is accomplished by implementing an output matching network which provides high impedance ‘open circuit’ to the odd harmonics and low impedance ‘shorts’ to even harmonics. This results in a squared off (though for Class-F, truly squared) voltage waveform. The third harmonic only is peaked.
- Class-F amplifiers are capable of high efficiency (88.4% for traditionally defined Class-F, or 100% if infinite harmonic tuning is used).

- Class-F amplifier design is difficult mainly due to the complex design of the output matching network.

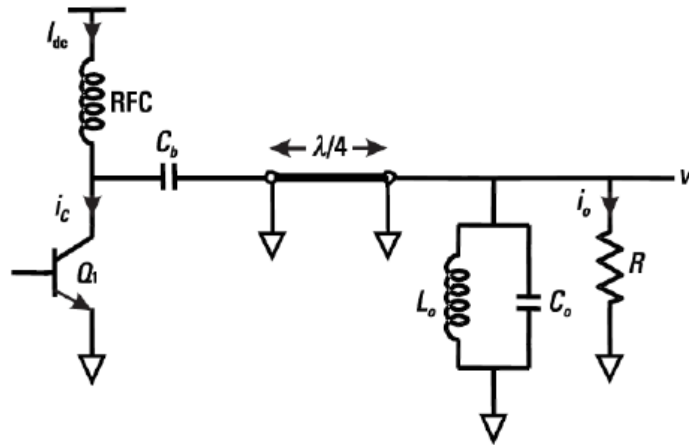A Class-F amplifier can also be built with a quarter-wave transmission line as shown below.




- A $\lambda/4$ transmission line transforms an open circuit into a short circuit and a short circuit into an open circuit.
- At the center frequency, the tuned circuit (L_o and C_o) is an open circuit, but at all other frequencies, the impedance is close to zero. Thus, at the fundamental frequency the impedance into the transmission line is RL .
- At even harmonics, the $\lambda/4$ transmission line leaves the short circuit as a short circuit.
- At odd harmonics, the short circuit is transformed into an open circuit. This is equivalent to having a resonator at all odd harmonics, with the result that the collector voltage waveform is a square wave (odd harmonics should be at the right levels).

Doherty Amplifiers

William H. Doherty invented this amplifier in 1936, for use in high-power AM broadcast transmitters. The technique dramatically improved the amplifier efficiency from about 30% to over 60%. The key gain device at the time was the vacuum tube, but the same approach is now applied to many different semiconductor technologies (CMOS, GaAs, LD MOSFET, and GaN).

The Doherty amplifier uses two amplifiers to optimize the overall PA performance. The carrier amplifier (or main amplifier) handles the low-power region while the peaking amplifier (or auxiliary amplifier) handles the high-power region. This sounds simple, but the practical implementation can be challenging. Figure below shows a classic Doherty amplifier with two amplifier paths, both fed from a hybrid coupler. The carrier amplifier is always on while the peaking amp remains idle unless the signal moves into the high-power region. In the high-power region, the peaking amp turns on and provides additional amplification to support the higher output power. Two important design challenges are 1) splitting and recombining the signal while maintaining time alignment 2) turning on the peaking amplifier under the proper conditions while maintaining linearity.

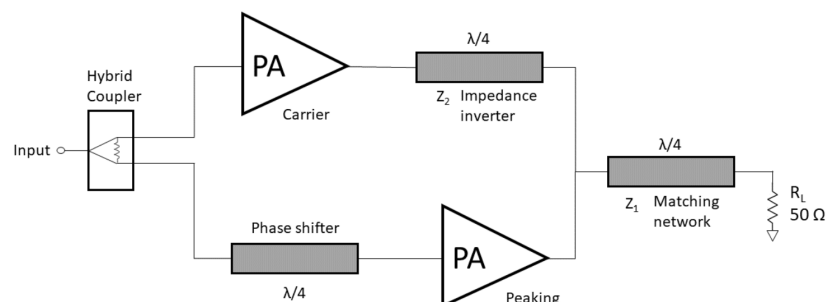

Send your technical subject of interest to IARS at iars.keithb@gmail.com

Memory lane, who built one of these?

DSE Radio Direction Finder

You cannot buy them anymore but with this information you should be able to build one.

Excerpted with permission from the February, 1986, issue of Electronics Australia.

Most readers will be broadly familiar with the concept of a radio direction finder (RDF). A basic RDF consists of a receiver and an antenna which can be rotated on its own axis. The direction of the transmitter is found by rotating the antenna for a signal peak or null.

You can easily demonstrate the effect for yourself using a portable transistor radio fitted with a ferrite rod antenna. By tuning the radio to a station and rotating the radio about its vertical axis, a null will be found in the signal strength. The ferrite rod antenna will then point in the direction of the station.

Of course, this method requires that "fixes" be taken at two or more widely spaced locations in order to find the true location of the transmitter. The exact location of the transmitter is determined by simple triangulation.

The classic application of this radio direction finding technique was in World War II. Many war movies showed how it was possible to track down enemy transmitters using special vans fitted with RDF equipment. Typically, these vans were fitted with a large external loop antenna which could be manu-

ally rotated. An operator inside the van listened in on headphones for peaks and dips in the signal strength. Provided the transmitter remained in the one location for long enough, its location could eventually be pinpointed.

The Dick Smith Radio Direction Finder is just the ticket for tracking down illegal transmitters and antisocial radio operators. Depending on the antenna system, it can operate on any band from 50 to 500 MHz and will work with FM receivers ranging from pocket scanners to amateur radio and CB transceivers.

Physically, the radio direction finder consists of two separate units. One contains the control and display electronics, and the other is a special antenna-switching unit (ASU) which is connected to the control unit via a 4-conductor cable.

An electronic "compass" display consisting of 32 LEDs indicates the transmitter bearing. When a signal is received, its relative bearing to the antenna system is indicated by whichever of the 32 LEDs illuminates.

In fixed installations, this allows the compass bearing of the signal to be directly indicated to within ± 5.6 degrees. When an RDF unit is installed in a car, successive readings allow you to pinpoint the exact location of the transmitter.

How It Works

The theory of operation is reasonably simple. Radio signals received on a rapidly moving antenna undergo a frequency shift due to the Doppler effect, an effect well known to anyone who has observed a moving car with its horn blowing.

Consider a single antenna mounted on the edge of a rapidly spinning disc (Fig. 1). As the antenna moves towards the source of the rf carrier, the apparent frequency will increase due to the Doppler effect (Fig. 2). Conversely, as the antenna moves away, the frequency will decrease.

Thus, the rotating antenna causes frequency modulation of the received carrier. When this type of antenna is connected to an FM receiver, a tone is heard. By analyzing the phase of this tone, the direction of the transmitter can be determined.

To avoid the obvious drawback of a mechanically rotated system, the Dick Smith RDF simulates a rotating antenna electronically. Four vertical whip antennas are arranged around a circle with a diameter of 0.07-0.4 wavelengths. The antennas are electronically switched clockwise in sequence such that all four antennas are scanned once every 1/1250th of a second.

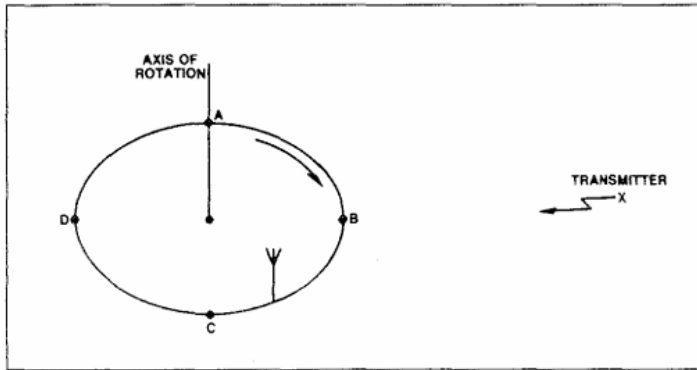


Fig. 1. Signals received by an antenna mounted on the edge of a rotating disc are frequency modulated due to the Doppler effect.

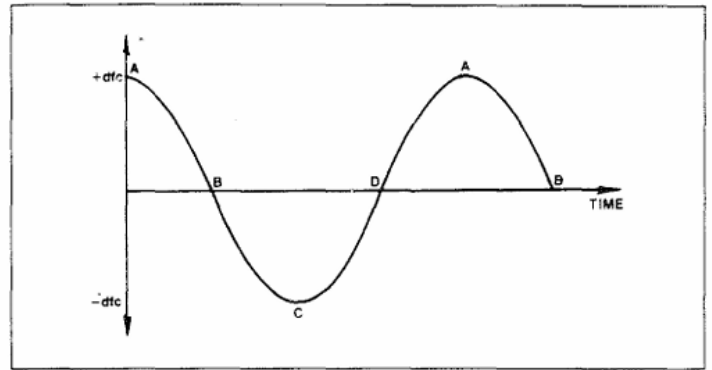


Fig. 2. This graph illustrates the frequency shift as the antenna moves towards and away from the transmitter.

This situation is equivalent to one vertical antenna mounted on the perimeter of a disc spinning at 1250 revolutions per second. A diameter of, say, 800 mm (for the 2-meter band) results in a tangential velocity of 3140 meters per second.

If the carrier frequency is 144 MHz, the carrier will deviate 1.5 kHz at a rate of 1250 Hz. For lower carrier frequencies, the deviation will be proportionally lower. Note, however, that the 1250-Hz modulating tone remains constant, as it is a function of the antenna switching rate only.

The output from the FM receiver is applied to the signal input of the RDF adapter and compared with an internal reference phase. The resultant phase angle appears as a 5-bit binary code which is decoded to a one-of-32 output to drive the appropriate LED indicator.

In addition, the detected audio tone can be monitored on an internal loudspeaker. This provides an audible indication that the receiver is correctly tuned to the transmitter frequency.

The Circuit

Antenna switching is accomplished by first deriving a 2-bit binary code from a 1-MHz master oscillator. Here's how it's done:

Inverter stages IC2a, b, and c (4069) form the 1-MHz oscillator, with buffering provided by IC2d. This clocks decade counters IC4 and IC7, both of which divide by five to produce a 40-kHz signal on pin 1 (CK) of IC10.


IC10 is a 4024 7-stage binary counter. Its Q1-Q5 outputs directly drive the D1-D5 inputs of IC12, a 40174 hex latch, while Q4 and Q5 also drive IC9, which is a 4555 one-of-four decoder.

What happens is that IC9 accepts a 2-bit binary code from IC10 and provides the quadrature antenna-switching signals. These signals are interfaced by a 1488 line driver (IC6). The outputs of IC6 swing positive and negative in sequence to provide bias for the matrix diodes (D201-D208) in the antenna-switching unit (ASU).

The diode matrix is arranged so that, at any given instant, three of the antennas are effectively shorted and only one is coupled to the receiver. For example, when pin 11 of IC6 is low (-9 V), D205-D207 are forward-biased and short out antennas 2 to 4. At the same time, D201 will also be forward-biased while D202-D204 are turned off. Antenna 1 will thus be connected to the receiver.

The detected audio tone from the FM receiver is applied to the input of the RDF adapter, limited by D1 and D2, and filtered by a single-pole active low-pass filter stage (IC5). This chip is described by National Semiconductor as an MF5 Universal Monolithic Switched Capacitor Filter. Basically, it is a general-purpose active-filter building block.

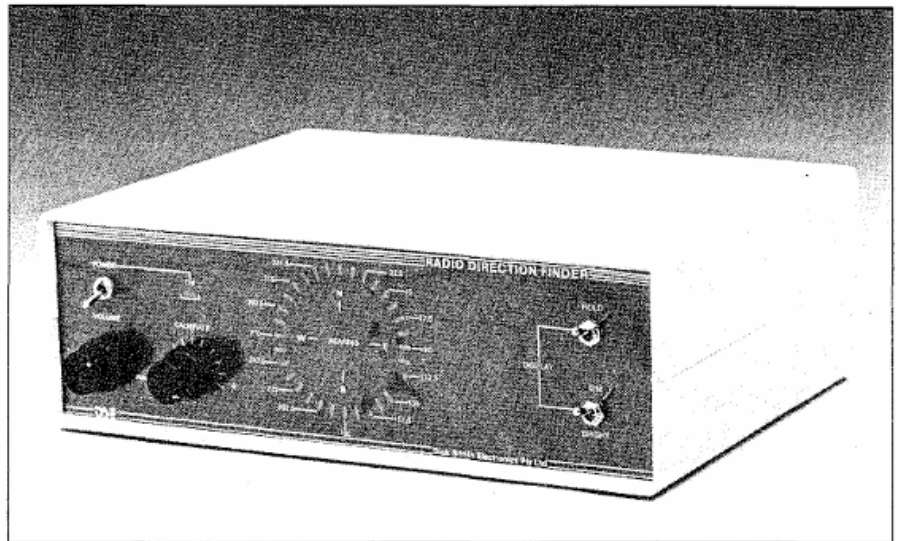The rest of IC5 is configured as a second-order bandpass filter to remove unwanted audio modulation from the 1250-Hz tone. The center frequency of the filter is set to



The Dick Smith Electronics Radio Direction Finder.

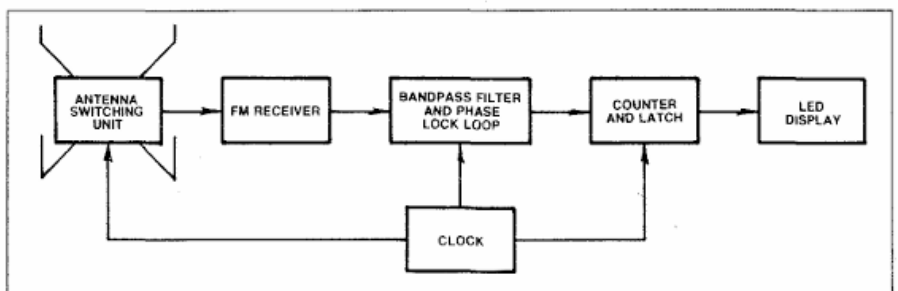


Fig. 3. Block diagram of the Radio Direction Finder. Signals from the antenna-switching unit are fed to an FM receiver and the output is compared to a reference phase.

1250 Hz by the clock signal applied to pin 8. This clock signal is derived via IC3, which divides the 1-MHz master oscillator signal by eight.

Note that the clock for the bandpass filter is derived from the same source as that used to switch the antennas. This means that the filter is automatically centered on the scanning tone, even when there is some frequency drift.

The output of IC5 (pin 1) is a sine wave with a nominal frequency of 1250 Hz. This signal is applied to op amp IC11a, which functions as a phase shifter. Adjustment of the phase shifter is by means of VR1.

The job of the phase shifter is to allow calibration of the circuit and to compensate for any audio phase shifts in the receiver.

From there, the signal is further processed by a 4046 phase-locked loop (PLL). The function of this stage is to average out any modulation present in the passband of IC5 and to produce a 1250-Hz square wave which is essentially free of noise and jitter.

It is this signal that is used to latch IC12. The output of the PLL (pins 3 and 4) is first inverted by IC2f and applied to D-type flip-flop IC13a. Subsequently, when the flip-flop's D input goes high, IC13a latches IC12 on the first positive-going clock pulse from pin 10 of IC4.

The result of all this is that IC12 is latched with a 5-bit code that is directly related to the

transmitter direction. A phase-comparator function is thus performed.

Note that IC13a is necessary to prevent the latching signal from coinciding with a change of data on IC12's inputs.

A pair of 74LS154 one-of-16 decoders (IC101 and IC102) on the display board converts the 5-bit code to a one-of-32 output. These decoders directly drive the 32 display LEDs to indicate that transmitter position.

Switch SW102 allows the display to be held or "frozen" by resetting IC13a. SW101 serves as a power on/off switch, while SW103 allows the display to be dimmed by switching a 330-Ohm resistor into the common anode circuit of the LED display.

To make the unit as easy as possible to use, the audio output from the FM receiver is also fed to an internal loudspeaker. The volume is adjusted by means of potentiometer VR102, which is mounted on the front panel.

Power Supply

Power for the RDF unit is derived from an external 12-V source which connects to a 2-conductor socket on the rear panel. This supplies +12 V direct to several ICs and to the input of 3-terminal regulator IC1. IC1, in turn, supplies a regulated +5-V rail to the remaining ICs.

Op amp IC11b provides a buffered +6-V rail to IC5 and also to the phase-calibration control (VR101).

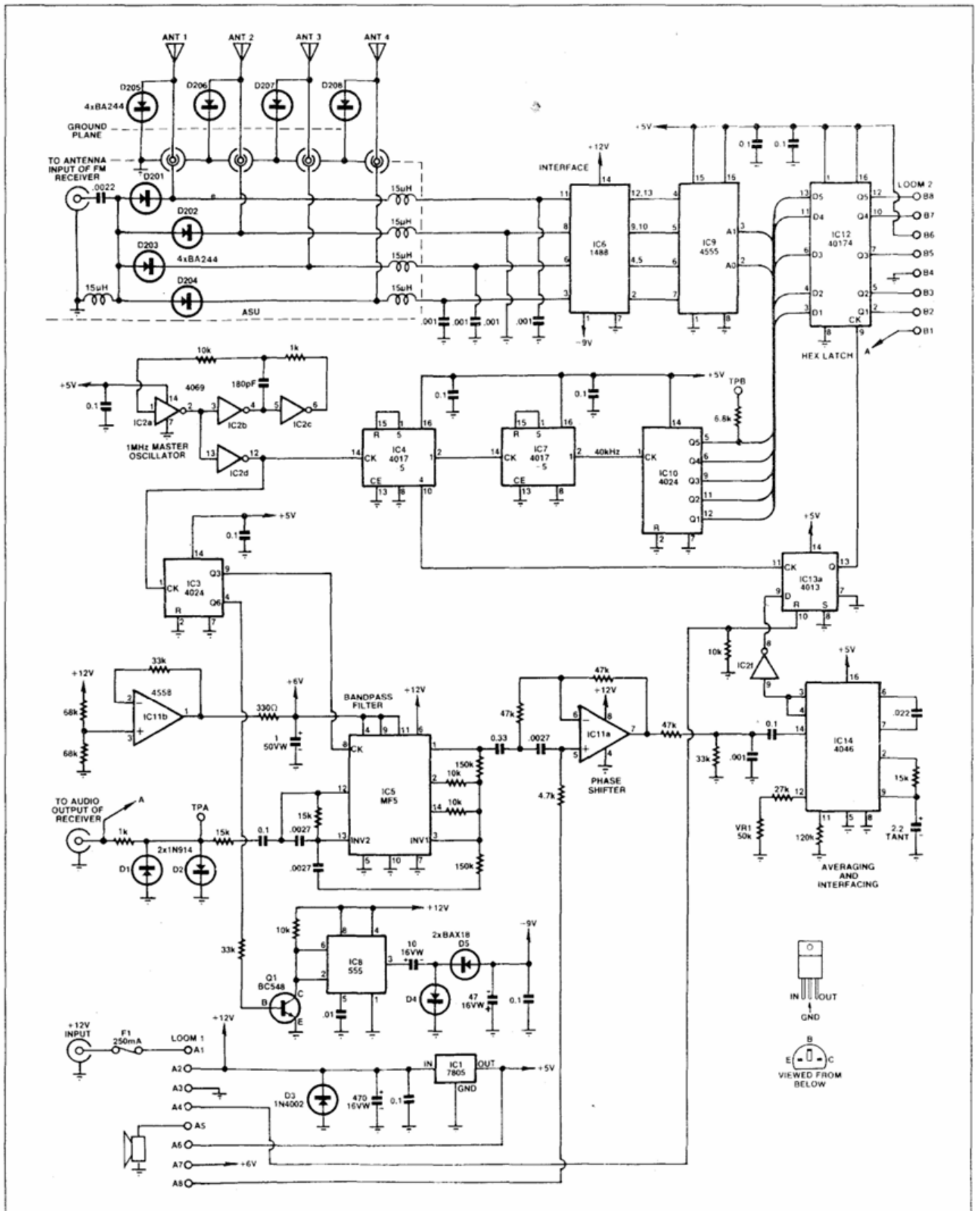


Fig. 4. The control and antenna-switching circuitry.

Finally, a -9-V supply rail is required for the 1488 line-driver IC. This is generated by a dc-to-dc converter circuit based on 555 timer IC8. It buffers a 16-kHz square wave derived from IC3 and drives a diode charge

pump based on D4 and D5 to produce the required -9-V rail.

Transistor Q1 simply functions as a switch. Its job is to interface the $+5\text{-V}$ CMOS circuit to the $+12\text{-V}$ timer circuit.

Construction

Construction is straightforward, with most of the parts mounted on three PC boards, two in the main unit and one in the ASU.

A plastic instrument case fitted with a per-

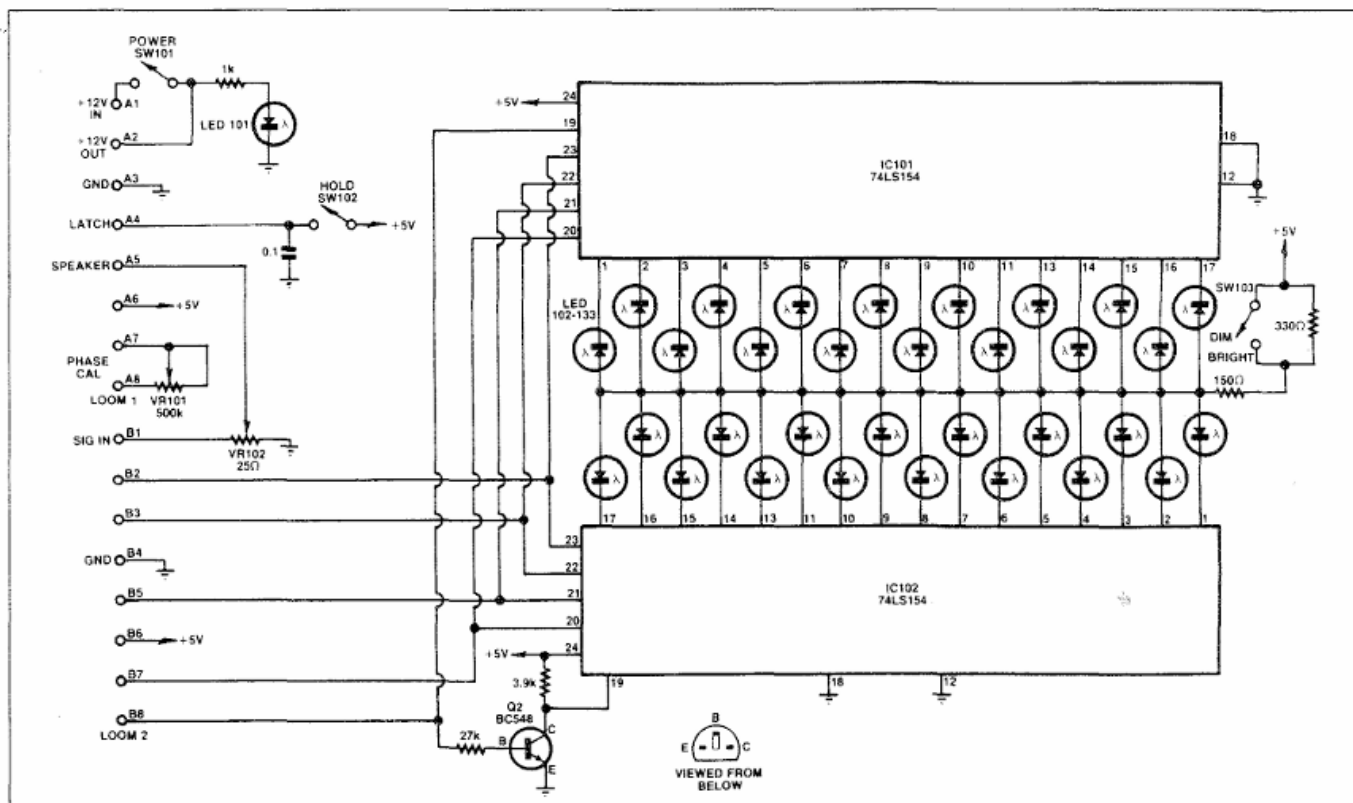


Fig. 5. The display circuit.

plex front panel houses the control electronics, while the ASU board is housed in a plastic project box.

Connections between the ASU and the control unit should be run using 4-conductor cable, while the connection to the FM receiver should be run using coaxial cable. All you have to do is trim the cables to the desired lengths and terminate them with the appropriate plugs.

Note that the wiring connections to the plugs at both ends of the control cable must be made on a one-to-one basis, otherwise the antennas will not rotate in the correct sequence.

Setting Up

An alligator clip lead and a small screwdriver are all that is necessary to adjust the unit.

Connect up a 12-V supply (be careful of polarity!) and switch on with the hold off and the ASU disconnected. All the LEDs in the display should rapidly flicker on and off as the display is scanned.

Assuming all is well, connect the two test points (TPA and TPB) together using the clip lead and adjust VR1 until a single LED is latched. Confirm this adjustment by unhooking and reconnecting the clip lead.

If the display does not latch when the test lead is reconnected, repeat the above procedure. This adjustment brings the vco to within the capture range of the PLL.

Note that, with the calibration control at mid-position, the latched LED should be the one at the top of the circle.

ANTENNAS AND OPERATION

For mobile operation, four 1/4-wave vertical whip antennas attached to a roof-rack assembly would be the best approach. The ASU could then be conveniently located between the antennas. It should be weather-proofed using a silicone sealant.

In most cases, a separate ground plane will have to be provided adjacent to the antenna bases. A suggested method is to secure a sheet of aluminum to the roof-rack. Make sure that the assembly cannot come loose!

A hand-held transceiver can be used to aid the initial setting-up procedure. Depending on the setup, it may be necessary to rotate the antenna array until the compass rose reads true relative to the direction of the vehicle.

The calibration control can be used to make the final adjustment. A walk around the antenna array with the hand-held transceiver will then reveal if the installation is functioning correctly. This should take place in an open area to avoid strong signal reflections.

In the case of a fixed installation, four ground-plane antennas should be mounted symmetrically on a vertical mast, together with the ASU. The array can then be adjusted so that the compass rose displays the true bearing with the calibration control set to mid-position.

Note that, in either case, the distance between opposing antennas should be between 0.07 and 0.4 wavelengths.

If a dual-trace oscilloscope is available, VR1 can be adjusted for a 90° phase angle between the signal input (pin 14, IC14) and the PLL comparator input (pin 3, IC14).

Finally, the control unit can be checked out by connecting outputs 1, 2, 3, and 4 (to the ASU) in sequence to test point TPA. First, connect output 1 to TPA and adjust the calibration control so that the latched LED is at 0°. The 90° LED should now light when output 2 is shorted, the 180° LED when output 3 is shorted, and the 270° LED when output 4 is shorted.

That completes the construction. Your Radio Direction Finder is now ready for use.

Where To Buy The Kit


The Radio Direction Finder described here was developed by the Research and Development Department at Dick Smith Electronics Pty Ltd. It is available as a complete kit of parts by mail order or from your nearest Dick Smith Electronics store.

The kit comes complete and includes a perspex front panel, screenprinted fiberglass PC boards, antenna bases, plugs and sockets, and a detailed construction manual. The cost is \$99 plus postage and packing charges where applicable.


Mail orders should be sent to: Dick Smith Electronics, PO Box 8021, Redwood City CA 94063; (800)-332-5373. ■

Fantastic Fox Finder from KIØHG—Construction Details



Hidden transmitter hunting, aka fox hunting, is a fun activity with serious overtones. Ideally it's a game, but the same equipment and skills can help find those in distress or track down a jammer. This post provides a schematic and construction details for a circuit developed by Dave Sharpe, KIØHG. His circuit below is by far the simplest direction finder I've run across. It works with two dipoles on a pole and provides a tone when the antenna array isn't quite pointed right, and nulls the tone when it is. I've used mine in many a two-meter fox hunt and it takes me right to the fox. Let's start with the schematic.

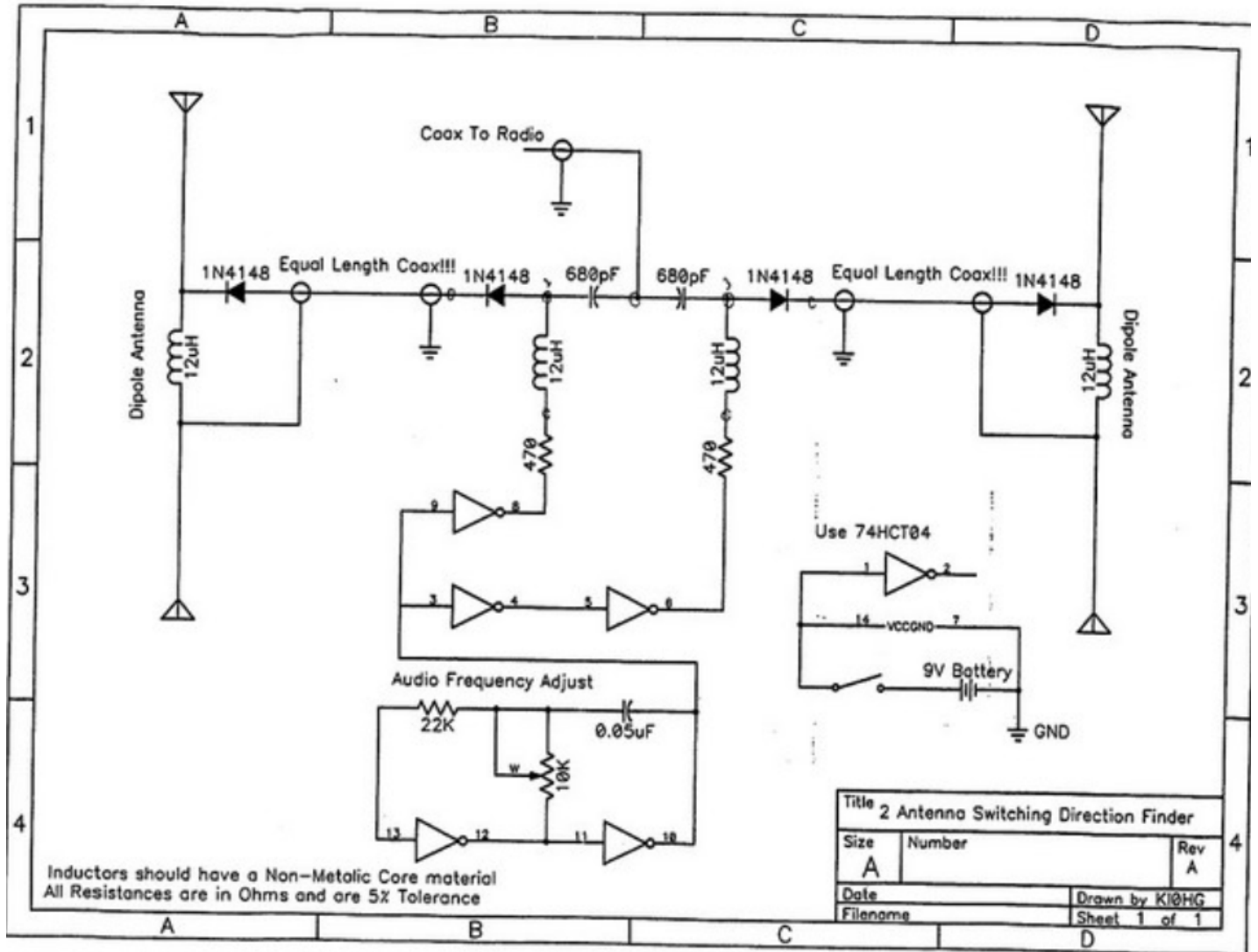

- The single IC is a 74HCT04, a CMOS hex-NOR-gate that takes very little current. Wire it as shown
- The audio tone is generated by two of the NOR-gates back to back with the 22K fixed resistor and the 10K potentiometer along with the .05µF capacitor.
- The diodes are all 1N4148 or 1N914 RF switching diodes. These are really inexpensive. The two in the middle go on the perf board along with the 680pF capacitors. The other two are at the very ends of the equal-length coax sections, as shown in the figure below

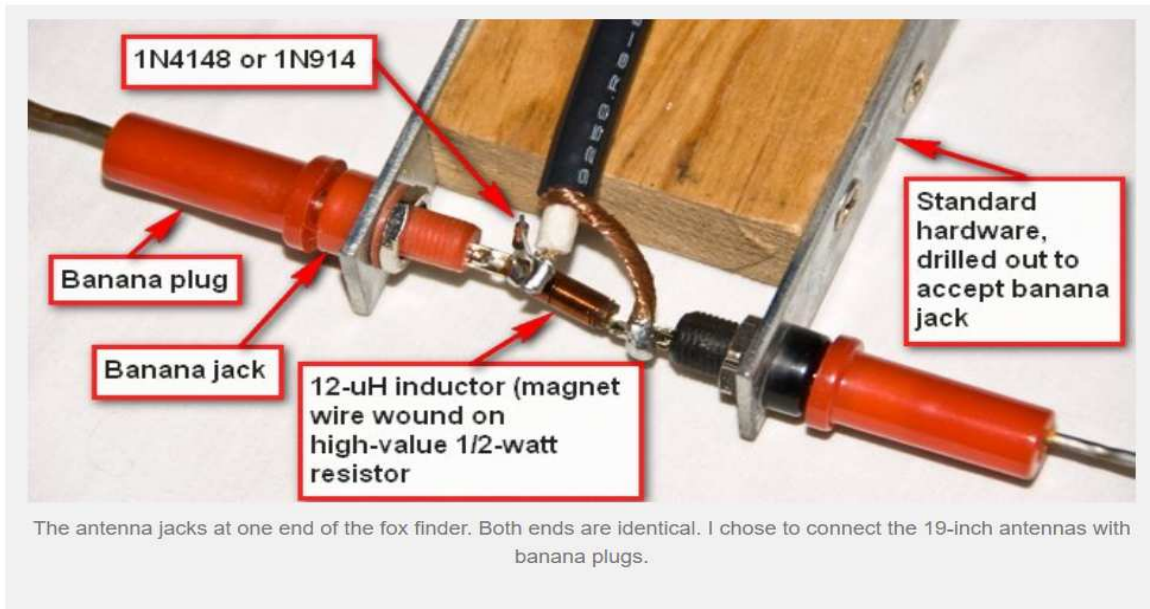

- The inductors can be store-bought, or can be made by winding magnet wire using a 1/2-watt high-value resistor—the old-fashioned cylindrical kind. The resistor should be greater than 100KΩ. The resistor is not important to the circuit.
- The pieces of coax from the circuit board to the antennas *must* be of the same length! Get this right, down to the millimeter!
- A Radio Shack perf board makes a great circuit board, as shown in the figure below.

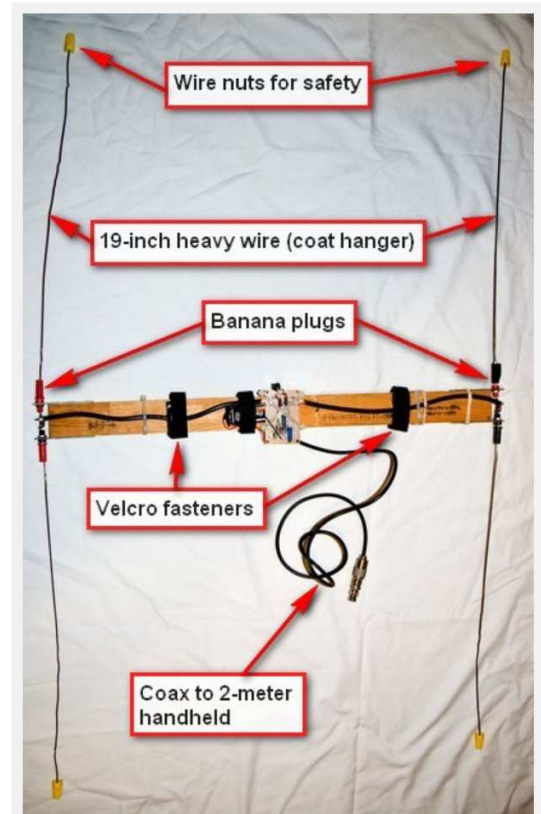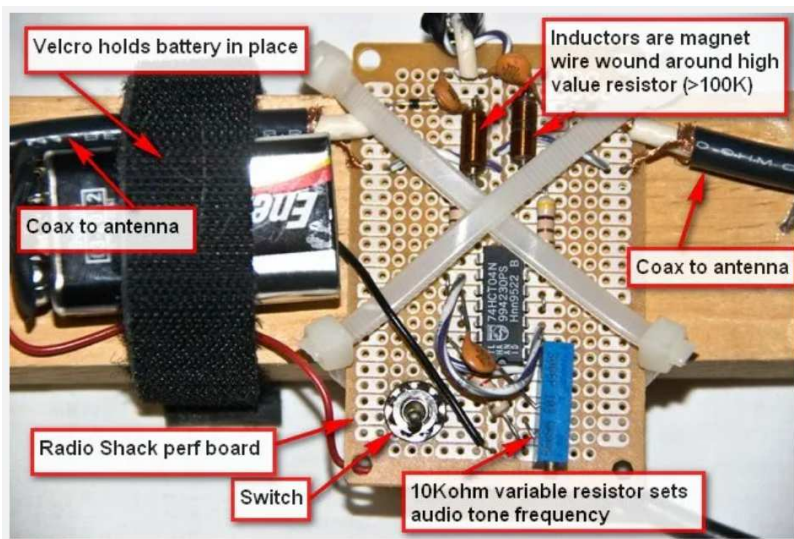

Parts:

- 12μH inductors, 1N4148 diodes, 470Ω resistors, 22KΩ resistors, 10KΩ potentiometer,
- 0.05μF capacitor, 680pF capacitors, 74HCT04 hex inverter,

Handy On Line Calculators

Send us your favourite handy calculator link so we can post it here!



Impedance <https://www.omnicalculator.com/physics/rlc-impedance>

Wavelength <https://www.omnicalculator.com/physics/wavelength>

PI attenuator values <https://www.omnicalculator.com/other/pi-attenuator>

Xc <https://www.omnicalculator.com/physics/capacitive-reactance>

XL <https://www.omnicalculator.com/physics/inductive-reactance>

Cut Off <https://www.omnicalculator.com/physics/cutoff-frequency>

VSWR <https://www.omnicalculator.com/physics/vswr-voltage-standing-wave-ratio>

LM317 Regulator resistor selector <https://www.omnicalculator.com/other/lm317>


Resistor Colour code calculator..... <https://www.digikey.com.au/en/resources/conversion-calculators/conversion-calculator-resistor-color-code>

Resistor Heat rise <https://calculator.academy/resistor-heat-calculator/>

Volt Drop Calculator AC and DC <https://www.rapidtables.com/calc/wire/voltage-drop-calculator.html>

NEW >>>> Helix antenna calculator <https://sgcderek.github.io/tools/helix-calc.html>

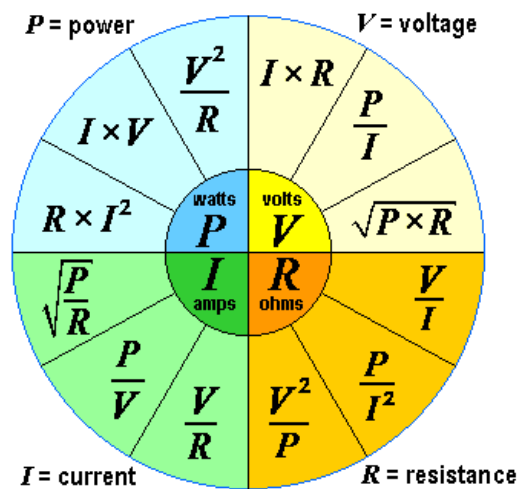NEW >>>> Parabolic dish calculator <https://www.everythingrf.com/rf-calculators/parabolic-reflector-antenna-gain>





How many of these can you answer correctly?

Question 1. A power amplifier has a gain of 20 dB. When fed with an input signal of 4 watts it will have an output of:

- (a) 80 watts
- (b) 400 watts
- (c) 200 watts
- (d) 24 watts

Question 2. To forward-bias a silicon-controlled-rectifier (SCR), the anode potential must be:

- (a) positive with respect to the cathode
- (b) negative with respect to the cathode
- (c) positive with respect to the gate
- (d) negative with respect to the gate

Question 3. The maximum reverse voltage that may be applied to a diode before the "avalanche breakdown" point is reached is called:

- (a) peak inverse voltage
- (b) cut-off voltage
- (c) saturation voltage
- (d) peak-to-peak voltage

Question 4. The bipolar transistor circuit configuration used to match high impedance to low impedance is the:

- (a) emitter follower
- (b) common base
- (c) common emitter
- (d) common source

Question 5. In a full-wave bridge rectifier, the peak inverse voltage rating of each of the four diodes must be:

- (a) low to ensure long life
- (b) rated at half the alternating voltage across the transformer secondary
- (c) equal to or exceed the rms value of the secondary voltage
- (d) more than 1.4 times the rms value of the secondary voltage

Question 6. A common collector (also called emitter follower) transistor amplifier has a voltage gain of:

- (a) less than one
- (b) greater than one
- (c) greater than 20
- (d) greater than 100

Answers next month 😊

Answers to last month's questions ... (Q1 = C ; Q2 = A ; Q3 = A ; Q4 = D ; Q5 = B ; Q6 = D)

How well did you do, will you still pass the Amateur Radio test?

Send your answers to iars.keithb@gmail.com to go into the draw for a prize at the end of the year

THE PROPAGATOR

THE MONTHLY NEWSLETTER OF THE
WIRELESS INSTITUTE OF AUSTRALIA
ILLAWARRA BRANCH

Published by the Illawarra Branch of
the Wireless Institute of Australia

P.O. Box 110
DAPTO 2530

No 6/75

JUNE 1975

No 6/75

PRESIDENT:

Keith Curle VK2ZYI
24 Beach Drive
WOONONA 2517

SECRETARY:

Ian Bowmaker VK2ZJA
15 Akuna Street
KEIRAVILLE 2500

NOTICE OF GENERAL MEETING

Members are advised that the next GENERAL MEETING of the Illawarra Branch of the W.I.A. will be held at the Wollongong Town Hall Committee Room on Monday, 9th JUNE 1975 at 7.30 p.m.

JUNE MEETING. GUEST SPEAKER.

This months meeting will be both interesting and important for all those concerned with Amateur Radio.

→ Our guest speaker is John Milton, VK2AQM, Wollongong District Radio Inspector, who will be talking on the subject of "Novice Licensing". This subject is of interest to Amateurs and Hobbyists alike, so bring your friends along to hear about our hobby and the way to become involved in it.

A raffle is to be held with a worthwhile and useful prize - so bring your money along. In the future we expect having tools, test equipment etc. as prizes in our raffles - this is to be the first of the upgraded raffles.

There is also an important matter of business to be discussed, so we urge all members to be present.

SUBSCRIPTIONS.

For those of you who have not forwarded your subscription, we must make this your last free issue of The Propagator. Because of increased postal rates and costs we are only able to send The Propagator to fully paid up subscribers.

So, if you have found The Propagator worthwhile reading and would like to continue receiving each issue, send in your subscription immediately.

The 1975 subscription rate is \$2, with concession rate of \$1 for students and pensioners.

Send to - The Secretary,

Illawarra Branch, W.I.A.,

PO BOX 110, DAPTO. 2530. N.S.W.

STORE.

The Committee has decided, after looking at a number of possible plans, to run the Store direct. We anticipate to be making purchases of selected components and offering these items for sale to readers of The Propagator. The components will be of prime quality and purchases will be made so that we can offer good savings when compared to the usual sources of component supply.

Elsewhere in this issue may be found details of components currently available.

Conditions of sale must be on the basis of -

CASH WITH ORDER

FIRST IN, FIRST SERVED

WHILE STOCKS LAST

BILL DIT KITSETS.

This the last and final notice for members who require parts to complete their Bill Dit Kitsets.

We must finalise the deal with our supplier by the end of June 1975.

All lists of outstanding parts must be in the hands of Bill VK2ZCO by the end of June otherwise this Branch cannot accept any responsibility for the obtaining of any outstanding components.

FOR SALE

1 only MR6A HIGH BAND F.M UNIT Complete with crystals for CHANNEL 1,4, and 8 . QQE03/12 FINAL , BLOCK FILTER
Also comes complete with an AC power supply \$35
GEOFF CUTBERT 22RU 2 NIOKA Av KEIRAVILLE 2500 Ph 289085

1 only MR10C converted for 92.525 but without crystals
Modified to remove handset control unit.
Volume and mute located on main unit \$20
GEOFF CUTBERT 22RU 2 NIOKA Av KEIRAVILLE 2500

Moonbounce Report - June.

Construction of the new one kilowatt power amplifier for the transmitter has been completed and it is now being installed in the main transmitter chassis.

Testing should be underway in about a week's time, after the required power supply wiring changes have been made.

Approx. 50 hours concentrated effort has gone into trying to get the transmitter operational again before the June series of IRE tests.

A letter has been received from FOPT who wants to arrange special IRE tests with VE2AMV.

The weekly 20 metre skeds with ZL5JJ continue to provide a useful interchange of IRE information.

It was noticed that an advertisement appeared in March QST for the new ARRL publication - 'Specialized Communication Techniques for the Radio Amateur' - and on the front cover of the book is a photograph of the Haplo Moonbounce installation! It will only cost you US\$3.00 to have a look. Hll

Lyle - VE2ALU.

Will share more oldies next month.

To read more information about this old propagator and others, use the link below

<https://www.iars.org.au/wp-content/uploads/2020/09/1975-06-June.pdf>

AR NEWS

CONSULTATION 2024-2: 40m Band Plan Harmonisation Challenges

Date : 09 / 07 / 2024
Author : Grant Willis VK5GR

CONSULTATION 2024-2: 40m Band Plan Harmonisation Challenges

The WIA as part of its involvement with IARU Region 3 is sponsoring a discussion on the future directions of the 40m band plan. It is now seeking feedback from members on a number of issues relating to the band to then use as input to the IARU Region 3 conference in October 2024.

The Amateur Service 7000-7200 kHz band is considered an example of one of the more dis-organised bands on a global basis.



Information link <https://www.wia.org.au/newsevents/news/2024/20240709-1/index.php>

CONSULTATION 2024-1: Australian Amateur Radio Repeater and Beacon Frequency Planning Rules and Process Changes

Date : 24 / 06 / 2024
Author : Grant Willis VK5GR

The WIA was first approached by the ACMA in 2022, to consider how improved transparency could be brought to Amateur repeater and beacon frequency selection processes. In addition, the ACMA wished to enable a pathway for obtaining an amateur spectrum repeater/beacon frequency assignment that did not require applicants to engage with the WIA directly if they didn't want to. The ACMA has released a consultation for the new process, including a new proposed Frequency Assignment Process document (FAP-10) in support of this (you can read about the ACMA part of the work here: <https://www.acma.gov.au/consultations/2024-06/amateur-repeater-and-beacons-assignment-process>)



More detailed information here <https://www.wia.org.au/newsevents/news/2024/20240624-1/index.php>

More information please use this link https://www.arnsw.org.au/html/page_tt.htm

Bendigo Amateur Radio & Electronics Club

Proudly presents the inaugural
BENDIGO RADIOFEST

Sunday August 18th 2024



East Bendigo Public Hall
35 Lansell Street
BENDIGO - Victoria

radiofest@barec.net.au

Fun Corner

Please send in your funnies to iars.keithb@gmail.com

Thanks to all that sent in funnies.

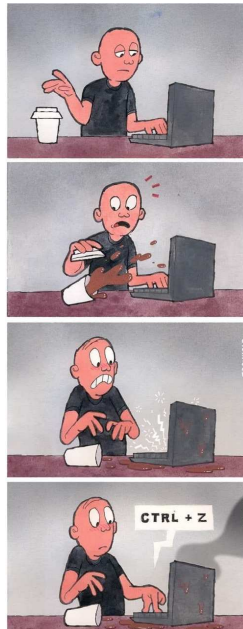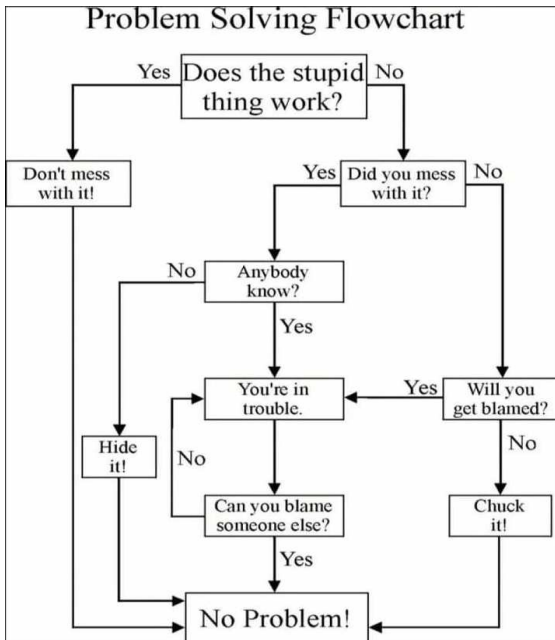

The IARS needs **YOUR** input and support, any technical items, amateur radio news, any projects you would like to share, in fact any AR related goings on are welcomed.

Feedback is also very important for us as it helps maintain a good read, if you would like to see more of something, or would like to see a subject added. Please let us know iars.keithb@gmail.com

That's all for now, hopefully catch you all at the **Blue Scope visitors centre on the 13th of August 7.30pm**

73
Keith VK2KQB
IARS Secretary

IARS, Amateur Radio in the Illawarra since 1948